

S.No. : 178

BCA2102

No. of Printed Pages : 04

Following Paper ID and Roll No. to be filled in your Answer Book.

| | | | | | | | | | | | | | | | | | | | | |
|-------------------------|-------------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| PAPER ID : 21102 | Roll No. | | | | | | | | | | | | | | | | | | | |
|-------------------------|-------------|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

BCA Examination 2018-19

(First Semester)

DIGITAL ELECTRONICS

Time : Three Hours]

[Maximum Marks : 60

Note : Attempt all questions. All questions are compulsory.

SECTION 'A'

1. Attempt all parts of the following : $1 \times 8 = 8$
 - (a) Convert octal number 475 to binary and decimal.
 - (b) Why NAND/NOR gates are called universal logic gate?
 - (c) Draw the logic diagram and truth table for half adder.
 - (d) Differentiate between decoder and multiplexer.

[P. T. O.

- (e) What is the significance of parity bit?
- (f) Write the characteristic equation for S R flip flop.
- (g) What is the difference between Synchronous and Asynchronous counters?
- (h) How many number of clock pulses required for serial data loading in an n bit register?

SECTION 'B'

Note : Attempt any two parts of the following : $6 \times 2 = 12$

- 2. (a) Write a note on error detecting and error correcting code.
- (b) Design full subtractor with truth table and logic diagram.
- (c) Explain race around condition in J. K flip flop and what is the condition to avoid it?
- (d) Explain Johnson counter with suitable diagram and truth table.

SECTION 'C'

Note :- Attempt all question from this section. Attempt any two parts from each question : $8 \times 5 = 40$

3. (a) Perform the following arithmetic operation :
- (i) Add 96 and 56 BCD numbers
 - (ii) Subtract 748 and 983 BCD number
- (b) Simplify the following boolean function's and implement the result using logic gate.
- $$f(A, B, C, D) = \sum m (0, 1, 2, 3, 11, 12, 14, 15)$$
- (c) Implement the following boolean function with NAND-NAND logic
- $$F = \overline{A} \overline{B} + \overline{A} C + \overline{B} C$$
4. (a) Design 4 bit binary to gray code converter.
- (b) Implement the following function using 8 :1 max
- $$f(A, B, C, D) = \sum m (0, 3, 5, 6, 10, 12)$$
- (c) Design full adder circuit using decoder.
5. (a) Explain in detail about J K flip flop. Also mention function, characteristic, excitation table for J K flip flop.
- (b) Explain master slave JK Flip Flop in detail and mention how race around condh is not present in this flip flop .

[P. T. O.

- (c) Convert S R flip flop to J K flip flop.
6. (a) Draw the neat circuit diagram of 4 bit ring counter and explain its working.
- (b) Explain how shift register works with the help of neat and clean diagram.
- (c) What is the difference between ring counter and Johnson's counter mention in detail.

